



ECEN Academy

www.ecenacademy.com


 - (91) 97908 73099

Analog Electronics Problem – 1

Instructions:

1. Do not discuss with any one while solving the problems
2. Do not use internet while solving the problems
3. Do not use books while solving the problems
4. Do not try to copy from others
5. Do the problems in an easy way.

Question 1: What is the V_o voltage?

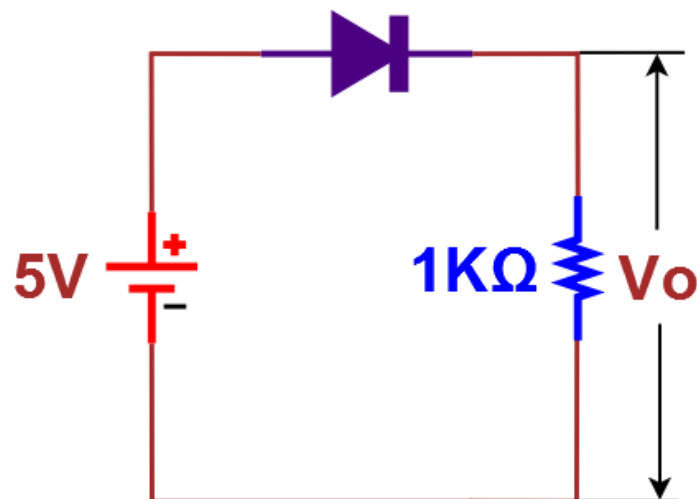

$$V = 5 - 0.7 = 4.3V$$
$$V = 4.3V$$



ECEN Academy

www.ecenacademy.com


 - (91) 97908 73099

Analog Electronics Problem – 2

Instructions:

1. Do not discuss with any one while solving the problems
2. Do not use internet while solving the problems
3. Do not use books while solving the problems
4. Do not try to copy from others
5. Do the problems in an easy way.

Question 2: What is the V_o voltage?

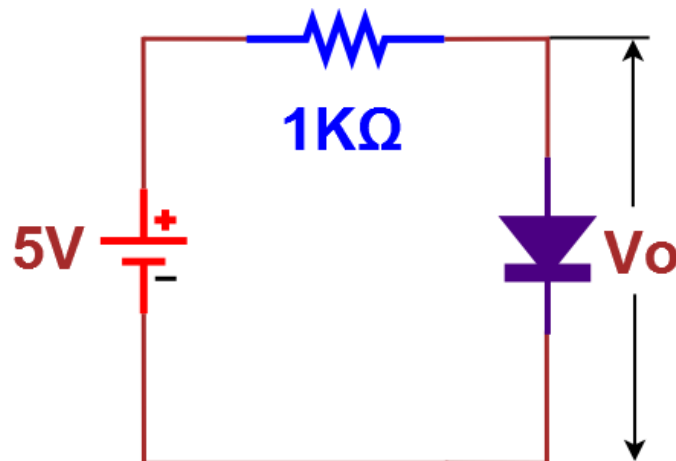

$V = 0.7V$
because voltage
across diode is 0.7v



ECEN Academy

www.ecenacademy.com


 - (91) 97908 73099

Analog Electronics Problem – 3

Instructions:

1. Do not discuss with any one while solving the problems
2. Do not use internet while solving the problems
3. Do not use books while solving the problems
4. Do not try to copy from others
5. Do the problems in an easy way.

Question 3: What is the V_o voltage?

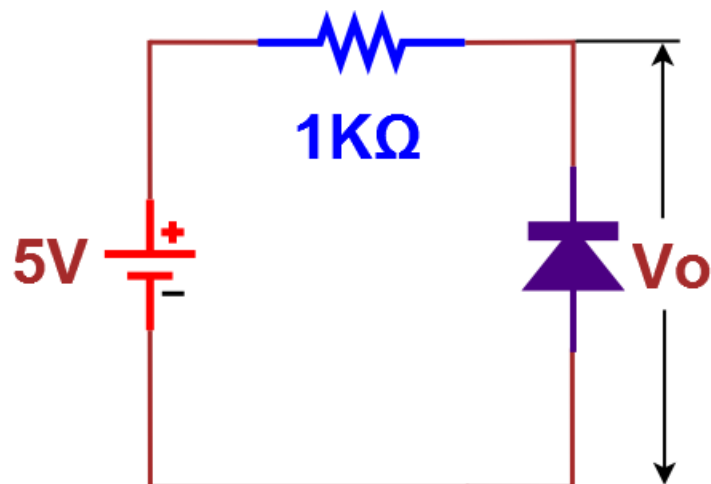


$$V = 5V$$



ECEN Academy

www.ecenacademy.com


 - (91) 97908 73099

Analog Electronics Problem – 4

Instructions:

1. Do not discuss with any one while solving the problems
2. Do not use internet while solving the problems
3. Do not use books while solving the problems
4. Do not try to copy from others
5. Do the problems in an easy way.

Question 4: What is the V_o voltage?

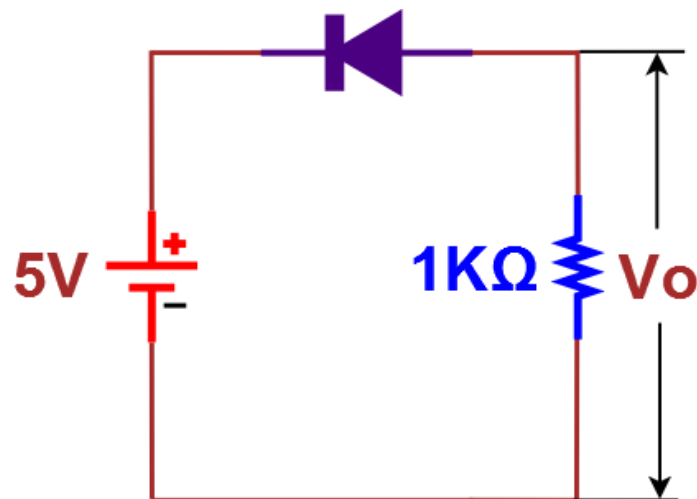


$V = 0$
because $I = 0$



ECEN Academy

www.ecenacademy.com


 - (91) 97908 73099

Analog Electronics Problem – 5

Instructions:

1. Do not discuss with any one while solving the problems
2. Do not use internet while solving the problems
3. Do not use books while solving the problems
4. Do not try to copy from others
5. Do the problems in an easy way.

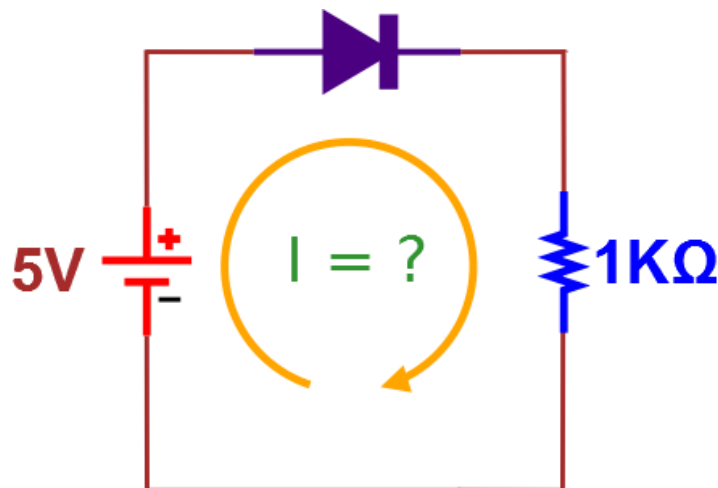Question 5: What is the value of Current I?



$$\begin{aligned} I &= V/R \\ I &= (5-0.7)/1K\Omega \\ I &= 4.3mA \end{aligned}$$



ECEN Academy

www.ecenacademy.com


 - (91) 97908 73099

Analog Electronics Problem – 6

Instructions:

1. Do not discuss with any one while solving the problems
2. Do not use internet while solving the problems
3. Do not use books while solving the problems
4. Do not try to copy from others
5. Do the problems in an easy way.

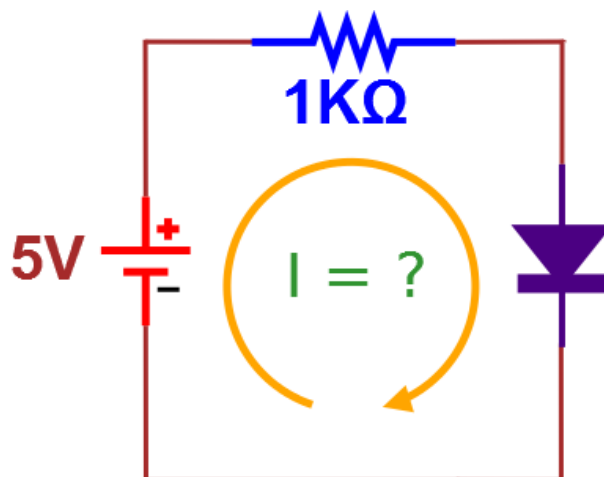Question 6: What is the value of Current I?




$$\begin{aligned} I &= V/R \\ I &= (5-0.7)/1K\Omega \\ I &= 4.3mA \end{aligned}$$



ECEN Academy

www.ecenacademy.com


 - (91) 97908 73099

Analog Electronics Problem – 7

Instructions:

1. Do not discuss with any one while solving the problems
2. Do not use internet while solving the problems
3. Do not use books while solving the problems
4. Do not try to copy from others
5. Do the problems in an easy way.

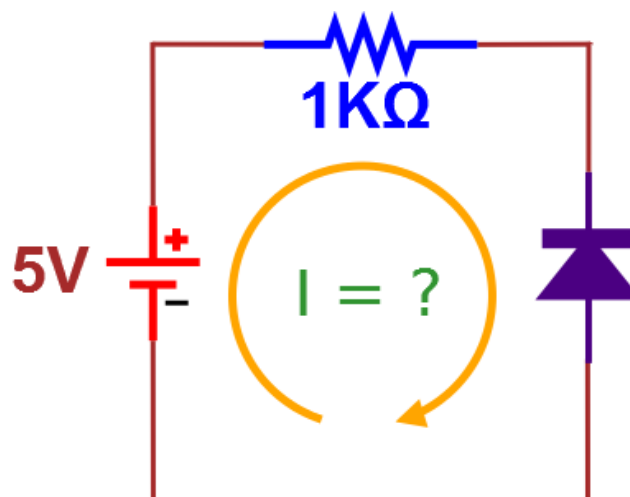Question 7: What is the value of Current I?



$I = 0$
because of diode



ECEN Academy

www.ecenacademy.com


 - (91) 97908 73099

Analog Electronics Problem – 8

Instructions:

1. Do not discuss with any one while solving the problems
2. Do not use internet while solving the problems
3. Do not use books while solving the problems
4. Do not try to copy from others
5. Do the problems in an easy way.

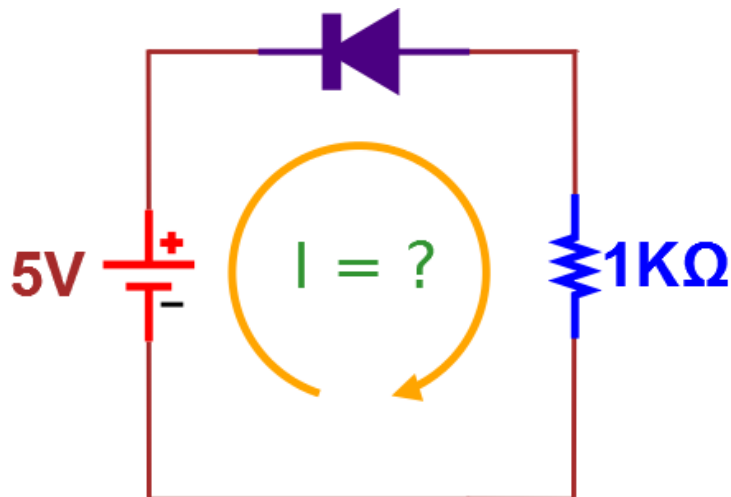Question 8: What is the value of Current I?



$I = 0$
because of diode



ECEN Academy

www.ecenacademy.com


 - (91) 97908 73099

Analog Electronics Problem – 9

Instructions:

1. Do not discuss with any one while solving the problems
2. Do not use internet while solving the problems
3. Do not use books while solving the problems
4. Do not try to copy from others
5. Do the problems in an easy way.

Question 9: What is the V_o voltage?

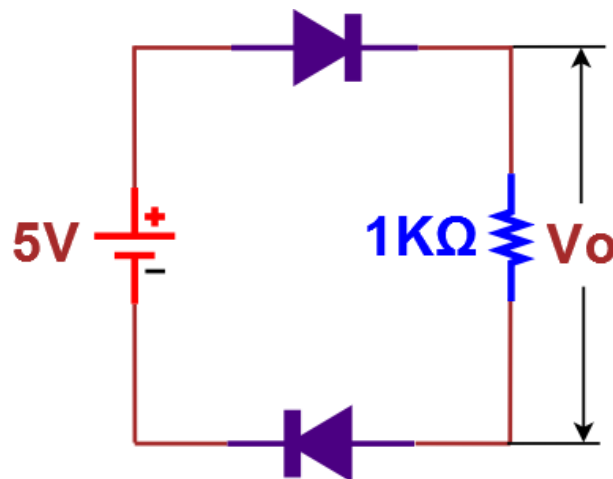

$$V = 3.6V$$



ECEN Academy

www.ecenacademy.com


 - (91) 97908 73099

Analog Electronics Problem – 10

Instructions:

1. Do not discuss with any one while solving the problems
2. Do not use internet while solving the problems
3. Do not use books while solving the problems
4. Do not try to copy from others
5. Do the problems in an easy way.

Question 10: What is the V_o voltage?

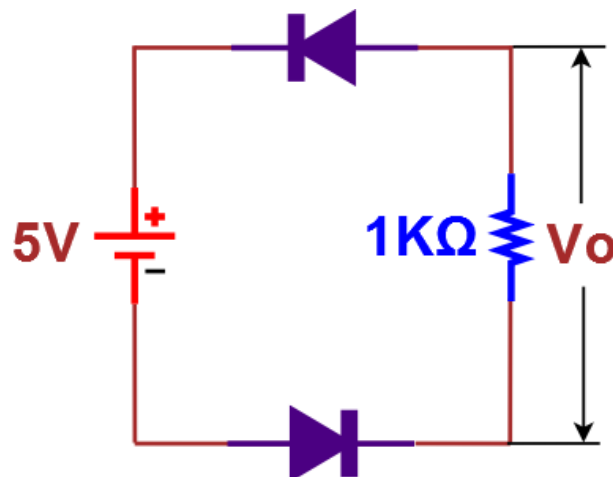

$$V = 0V$$