
www.ecenacademy.com (91) 97908 73099

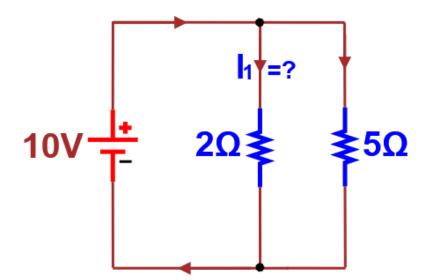

## <u>Electrical Problem – 31</u>

### Instructions:

- 1. Do not discuss with any one while solving the problems
- 2. Do not use internet while solving the problems
- 3. Do not use books while solving the problems
- 4. Do not try to copy from others
- 5. Do the problems in an easy way.



I = V/R

I = 10/2


I = 5A

www.ecenacademy.com (91) 97908 73099



## <u>Electrical Problem – 32</u>

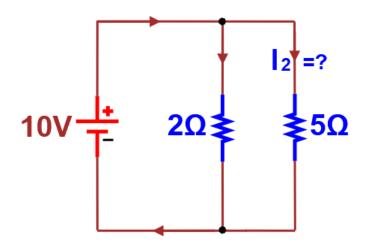- 1. Do not discuss with any one while solving the problems
- 2. Do not use internet while solving the problems
- 3. Do not use books while solving the problems
- 4. Do not try to copy from others
- 5. Do the problems in an easy way.



$$I = V/R$$
  
 $I = 10/5$ 


$$I = 2A$$

www.ecenacademy.com



## <u>Electrical Problem – 33</u>

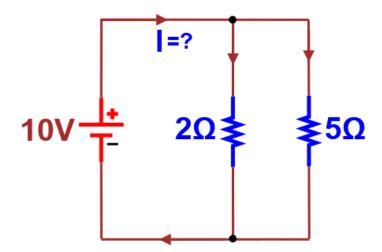- 1. Do not discuss with any one while solving the problems
- 2. Do not use internet while solving the problems
- 3. Do not use books while solving the problems
- 4. Do not try to copy from others
- 5. Do the problems in an easy way.




## www.ecenacademy.com



### **Electrical Problem – 34**

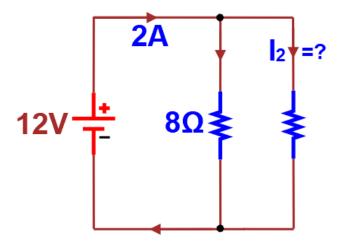- 1. Do not discuss with any one while solving the problems
- 2. Do not use internet while solving the problems
- 3. Do not use books while solving the problems
- 4. Do not try to copy from others
- 5. Do the problems in an easy way.






www.ecenacademy.com



### **Electrical Problem – 35**

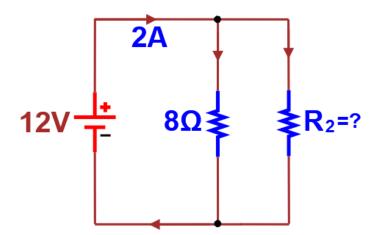- 1. Do not discuss with any one while solving the problems
- 2. Do not use internet while solving the problems
- 3. Do not use books while solving the problems
- 4. Do not try to copy from others
- 5. Do the problems in an easy way.




$$I = V/R$$
  
 $2 = 12/(8*R/8+R)$   
 $8R = 48+6R$   
 $2R = 48$   
 $R = 24\Omega$ 

www.ecenacademy.com (91) 97908 73099



### **Electrical Problem – 36**

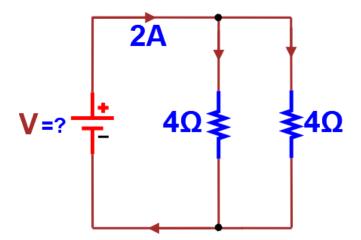- 1. Do not discuss with any one while solving the problems
- 2. Do not use internet while solving the problems
- 3. Do not use books while solving the problems
- 4. Do not try to copy from others
- 5. Do the problems in an easy way.



$$V = I*R$$

$$V = 2*2$$


$$V = 4V$$

www.ecenacademy.com



### <u>Electrical Problem – 37</u>

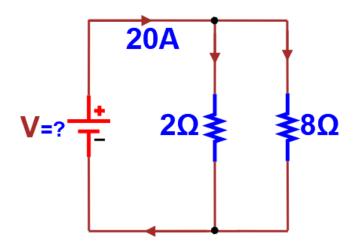- 1. Do not discuss with any one while solving the problems
- 2. Do not use internet while solving the problems
- 3. Do not use books while solving the problems
- 4. Do not try to copy from others
- 5. Do the problems in an easy way.



$$V = I*R$$

$$V = 20*(2*8/2+8)$$
  
 $V = 12.5V$ 

$$V = 12.5V$$


www.ecenacademy.com



### **Electrical Problem – 38**

#### Instructions:

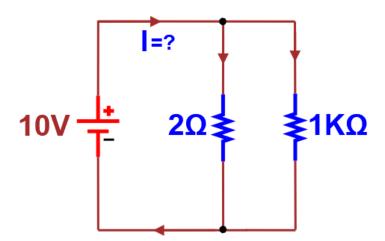- 1. Do not discuss with any one while solving the problems
- 2. Do not use internet while solving the problems
- 3. Do not use books while solving the problems
- 4. Do not try to copy from others
- 5. Do the problems in an easy way.



I = V/R

I = 10/1.996

I = 5.01A




## www.ecenacademy.com



### **Electrical Problem – 39**

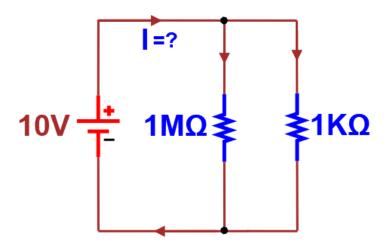- 1. Do not discuss with any one while solving the problems
- 2. Do not use internet while solving the problems
- 3. Do not use books while solving the problems
- 4. Do not try to copy from others
- 5. Do the problems in an easy way.




www.ecenacademy.com



### **Electrical Problem – 40**

### Instructions:

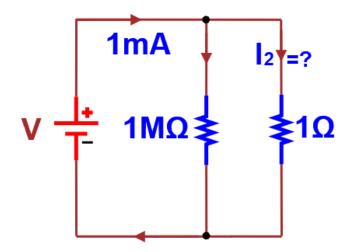- 1. Do not discuss with any one while solving the problems
- 2. Do not use internet while solving the problems
- 3. Do not use books while solving the problems
- 4. Do not try to copy from others
- 5. Do the problems in an easy way.



V = I\*R

V = 0.001\*1

V = 0.001V

I = V/R

I = 0.001/1

I = 1mA